

ENPH 253 Introduction to Instrument Design
www.engphys.ubc.ca/enph253



Instruction: Andre Marziali, Jon Nakane
 Technical: Bernhard Zender
 TAs: Matt Lam, Rob Stead, Yegor Rabets

1

Focus in ENPH 253

- Basic electronics, mechanical design
- Prototyping skills
- Independent design

- Practical problem-solving
- Team work
- Prioritization of time, team effort
- Estimating time, effort for technical tasks

2

Tinkering vs. Design

3

Schedule

First six weeks:

Lecture: Tue 2:00 – 5:00 IKBLC 182
Lab: Thurs 2:00 - ? (typically 9:30) Hebb 42

After week 6:

Lab: Tue & Thurs 2:00 – 10pm
 + additional days and evenings as required.

Machine Shop Course

ALL STUDENTS take the machine shop course (10 hrs + lecture) if they have not completed the 40-hour shop course.

10-hr course for groups of 6 held on two afternoons (M/W/F), sign-up during Lab 1

Wed May 9, 1pm-3pm, Hennings 201 (attendance required for all students)

Machine Shop Intro and Safety

Fri May 11, 1pm-2:30pm, Hennings 201 (attendance required for all students)

Intro to Solidworks (Bernhard Zender)

4

Formal Labs (6 weeks)

- 1 – Microcontrollers and digital I/O
- 2 – Analog circuits and I/O
- 3 – PWM and Power circuits
- 4 – Mechanical Design
- 5 – PID control and tape following (2 weeks)

Design and design review (1 week)
Construction (6-7 weeks)
Individual time-trials ~week 12

Competition: Thurs Aug 2nd, 10am
Cleanup Friday Aug 3rd, 10am
Final Report Friday August 10th

5

Team Mark

Competition results	25%
Robot design / construction:	30%
Individual time-trials:	25%
Design Review	20%
Inappropriate lab practice	Max -20%
(parts hoarding, unsafe practice, messy space, etc)	

Individual Mark

Team self evaluation:	± 10%
Lab performance:	± 20%

6

References

There is no required text. Lecture notes, labs and data sheets will be posted on web page:

- refer to Wiring programming website (wiring.org.co)
- **Horowitz and Hill**, Sedra and Smith
- MIT 2.007 Course Notes (link on course website)
- Online Component Vendors (Newark, McMaster)

Logbooks

necessary for labs & construction, but not marked

Circuit drawing and simulation

<https://www.circuitlab.com/editor/>

7

Class Activities

- Most “Teaching” will be done through in-class activities.
- Try to build circuit that we suggest
- Once you are successful, help people around you.
- Do not just build it for them. Explain how you did it instead.
- Bring laptop or smartphone

8

Ph253 final 2012:

ENPH 253 – Introduction to Instrument Design
projectlab.engphys.ubc.ca/enph253
Competition Rules

summer 2012


Block Stacking-Bots – are you faster than a pre-schooler?



Vs.



9

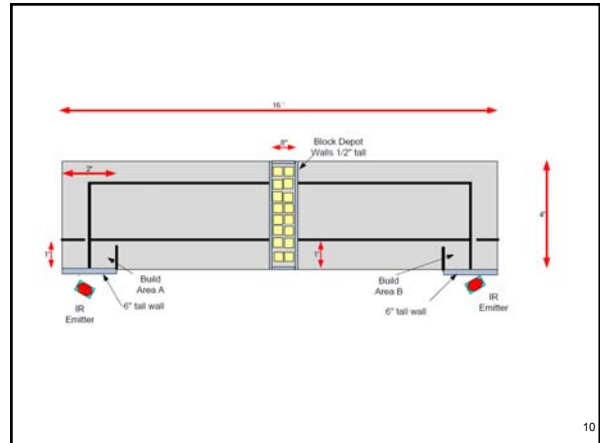

10

“Smart” instruments


The use of microprocessors to replace mechanical systems leads to

- better performance
- higher reliability
- more complex behavior with a mechanically simpler instrument
- often lower total cost of instrument

Eg #1: mechanical vs. electronic thermostats








“Smart” instruments

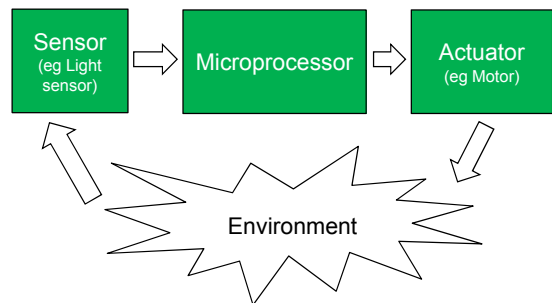

Rescue bot video

13

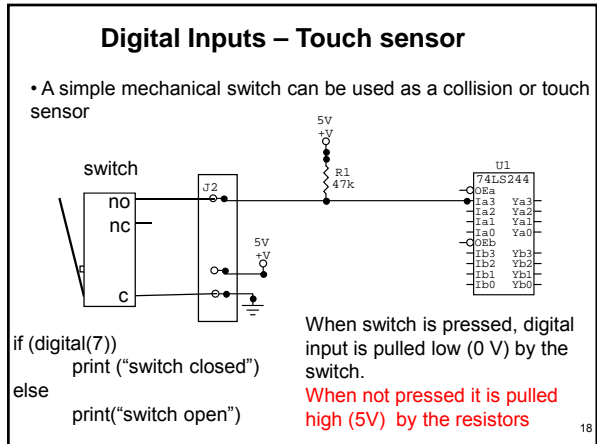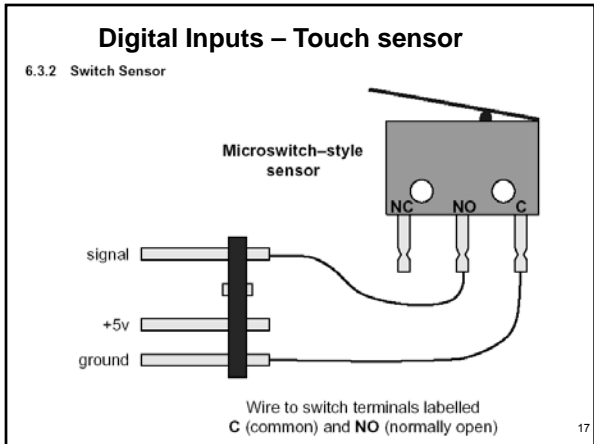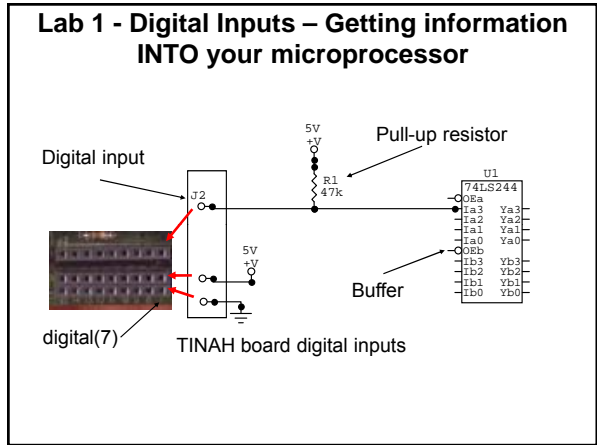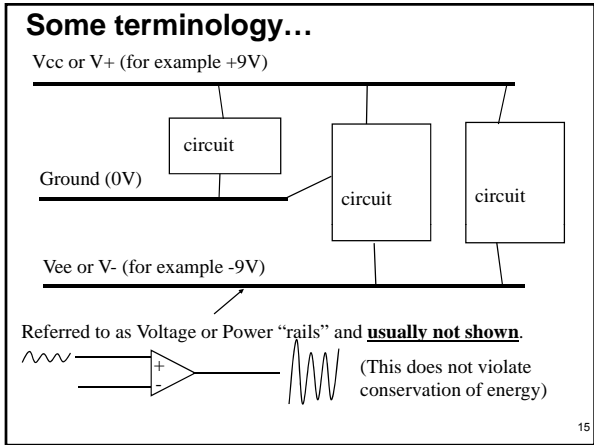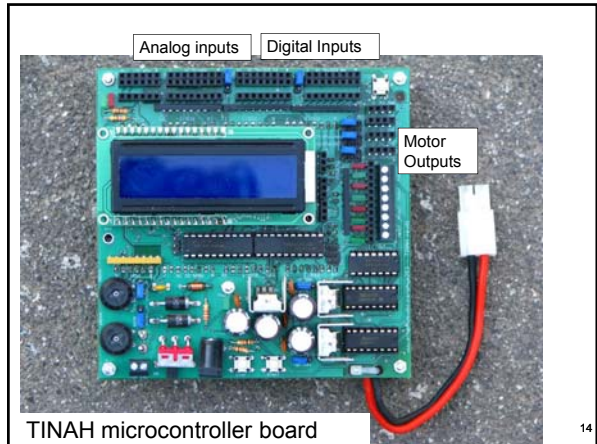


Digital Inputs – Touch sensor

Build a circuit that has:

- An LED that is normally lit
 - While a switch is pressed, the LED goes off
- ❖ Note: LED can only handle ~ 100 mA
- ❖ Design this so the battery is not badly drained when the switch is pressed
- ❖ If the battery or LED is getting hot, you're doing something wrong

Digital Inputs – Touch sensor

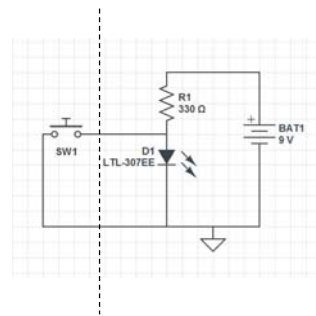

Digital Inputs – Touch sensor

```
#include <phys253.h>
#include <LiquidCrystal.h>
#include <Servo253.h>

////////////////////////////////////
// Physics 253 - Lecture 1
// 2009 May 4
////////////////////////////////////

void setup()
{
  while(!startbutton())
  {
    LCD.clear(); LCD.home();
    LCD.print("Welcome to 253!");
    delay(1000);
    LCD.clear(); LCD.home();
    LCD.print("Come down to");
    LCD.setCursor(0,1); LCD.print("pickup
    kits...");
    delay(1000);
  }
}


void loop()
{
  while (!stopbutton())
  {
    LCD.clear(); LCD.home();
    if (digitalRead(0))
    { LCD.print("switch pressed."); }
    else
    { LCD.print("switch NOT pressed."); }
    delay(100);
  }

  while (!startbutton())
  {
    LCD.clear(); LCD.home();
    if (digitalRead(0))
    { LCD.print("object detected."); }
    else
    { LCD.print("object NOT detected."); }
    delay(100);
  }
}
```

21

LM311 comparator – open collector output

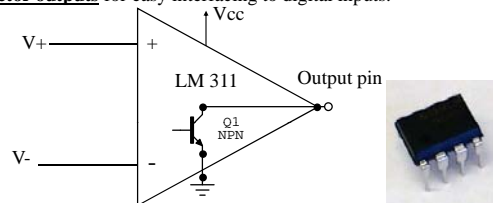- Comparators and other chips are sometimes provided with Open Collector outputs for easy interfacing to digital inputs.



When $V+ < V-$, Q1 is turned on (conducting). Output pin is grounded through Q1. When $V+ > V-$, Q1 is off, and output pin floats unless externally pulled up!!! (but Q1 cannot sink any current to ground).

Remember: it takes very little charge to change the voltage of a disconnected wire!

22

LM311 comparator – Example of a data sheet

5.0 Absolute Maximum Ratings for the LM311 (Note 12)

If Military/Aerospace specified devices are required, please contact the National Semiconductor Sales Office/Distributors for availability and specifications.


Total Supply Voltage (V_{DD})	36V	Operating Temperature Range	0° to 70°C
Output to Negative Supply Voltage (V_{OL})	40V	Storage Temperature Range	-65°C to 150°C
Ground to Negative Supply Voltage (V_{-})	30V	Lead Temperature (soldering, 10 sec)	260°C
Differential Input Voltage	±30V	Voltage at Strobe Pin	V ⁻ -5V
Input Voltage (Note 13)	±15V	Soldering Information	
Power Dissipation (Note 14)	500 mW	Dual-In-Line Package	
ESD Rating (Note 19)	300V	Soldering (10 seconds)	260°C
Output Short Circuit Duration	10 sec	Small Outline Package	
		Vapor Phase (60 seconds)	215°C
		Infrared (15 seconds)	220°C

DANGER LEVELS: Exceeding these voltages / currents will blow up the chip.

23

LM311 comparator – Example of a data sheet

11.0 Connection Diagrams

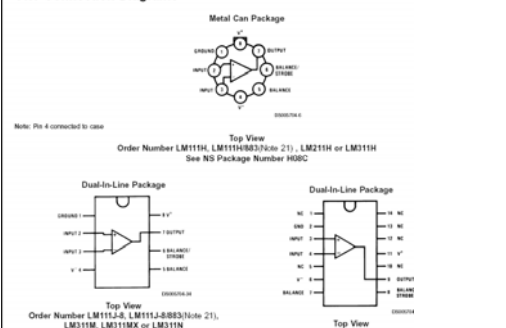

The most often used page – how to hook up the chip.

24

LM311 comparator – Example of a data sheet

Electrical Characteristics (Note 15) for the LM311

Parameter	Conditions	Min	Typ	Max	Units
Input Offset Voltage (Note 16)	$T_A=25^\circ\text{C}$, $R_{G1}=50\text{k}$		2.0	7.5	mV
Input Offset Current (Note 16)	$T_A=25^\circ\text{C}$		5.0	50	nA
Input Bias Current	$T_A=25^\circ\text{C}$		100	250	nA
Voltage Gain	$T_A=25^\circ\text{C}$	40	200		V/mV
Response Time (Note 17)	$T_A=25^\circ\text{C}$		200		ns
Saturation Voltage	$V_{IH}=10\text{ mV}$, $I_{OL1}=50\text{ mA}$ $T_A=25^\circ\text{C}$		0.75	1.5	V
Strobe ON Current (Note 18)	$T_A=25^\circ\text{C}$		2.0	5.0	mA
Output Leakage Current	$V_{IH}=10\text{ mV}$, $V_{OL1}=35\text{V}$ $T_A=25^\circ\text{C}$, $I_{B1(OL1)}=3\text{ mA}$ $V_I = \text{Pin 1} = -5\text{V}$		0.2	50	nA
Input Offset Voltage (Note 16)	$R_{G1}=50\text{k}$			10	mV
Input Offset Current (Note 16)				70	nA
Input Bias Current (Note 16)				300	nA
Input Voltage Range		-14.5	13.8-14.7	13.0	V
Saturation Voltage	$V_I=4.5\text{V}$, $V_I=0$		0.23	0.4	V
Positive Supply Current	$T_A=25^\circ\text{C}$		5.1	7.5	mA
Negative Supply Current	$T_A=25^\circ\text{C}$		4.1	5.0	mA


Important operating characteristics: these numbers will tell you how the chip will behave.

25

LM311 comparator – Example of a data sheet

7.0 LM311 Typical Performance Characteristics


Output Saturation Voltage

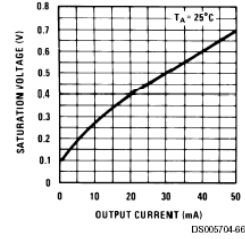

LM 311 can only sink a limited amount of current

26

LM311 comparator – open collector output

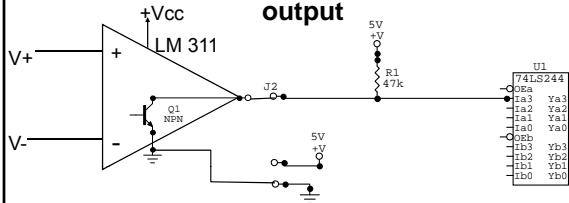

Unlike an OP-amp, the 311 is NOT a source of power! You cannot drive a load with the output pin.

Now, when Q1 is off, digital input J2 is pulled high by R1. When Q1 is on, J2 is pulled low (~0.1 or 0.2 V) by Q1. Note that the LM311 and the TINAH must share ground for this to work, but DO NOT NEED TO SHARE POWER RAILS.

27

LM311 comparator – open collector output


Build a circuit that has:

- An LED that is normally lit
 - While a switch is pressed, the LED goes off
 - The LED is connected to switch through a 311
- ❖ Note: Can use both batteries or only one

28


LM311 comparator – open collector output

Start with this circuit and fill in:

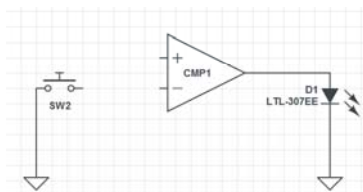

29

LM311 comparator – open collector output

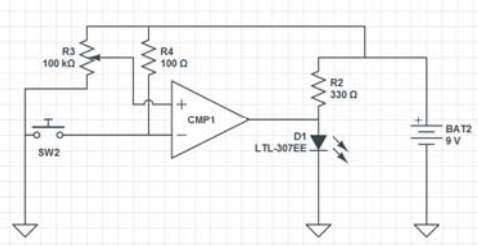

30

Example: QRD1114 reflectance sensor

QTD
OPTOELECTRONICS

QRD1113/1114 REFLECTIVE OBJECT SENSOR

PACKAGE DIMENSIONS

FEATURES

- Photometer Output
- No contact surface sensing
- Unobscured for sensing diffused surfaces
- Compact Package
- Daylight filter on sensor

NOTES

(Applies to Max Ratings and Characteristics Tables.)

1. Derate power dissipation linearly 1.33 mW/°C above 25°C.
2. ESDA flux is recommended.
3. Maskcoat or isopropyl alcohol are recommended as cleaning agents.
4. Soldering iron use (1 second from housing).
5. As long as leads are not under any spring tension.
6. D is the distance from the sensor face to the reflective surface.
7. Current $I_{C(d)}$ is the collector current measured with the indicator current on the input diode and with no reflective surface.
8. Measured using an ESDAtron Kodak neutral white test card with 90% diffused reflecting on a reflective surface.

NOTES:

1. Dimensions for all drawings are in inches (millimeters).
2. Tolerance of a .010 (.25) on all non-circular dimensions unless otherwise specified.
3. Pins 2 and 4 typically .005" shorter than pins 1 and 3.
4. Dimensions controlled at housing surface.

SCHEMATIC

31

Example: QRD1114 reflectance sensor

Build a circuit that has:

- An LED that is normally lit
- When your finger comes near the QRD sensor, the LED goes off

- ❖ Note: Use a comparator
- ❖ Note: Use a potentiometer to allow you to vary the threshold distance of your finger to the sensor

32

Example: QRD1114 reflectance sensor

33

Discrete devices: diodes

Standard diode symbol

P-type end N-type end

$\Delta V = 0.7 V$
Treat as conductor

$I = 0 A$
Treat as open circuit

Typical $\sim 0.7 V$

34

Diagrams courtesy of: University of St. Andrews, St Andrews, Fife KY16 9SS, Scotland

Discrete devices: diodes

Build a circuit that has:


- A lamp that is lit
- When you reverse the battery polarity the lamp goes off

35

Discrete devices: diodes

36

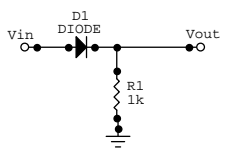$V_{in} = 5V$ DC, V_{out} is connected to scope only.



a) $V_{out} = 5V$ if $R1 = 1K$
 b) $V_{out} = 4.3V$ regardless of $R1$
 c) $V_{out} = 4.3V$ if $R1 = 1K$
 d) $V_{out} = 5V$ if $R1$ is removed
 e) $V_{out} = 4.3V$ if $R1$ is removed

The following are true: (Try it with your own meter)

- a
- b,c,e
- c,d
- a,e
- c

37

Discrete devices: Transistors

Transistors are semiconductor devices used to **amplify** a signal (e.g. small current/voltage to large current/voltage).

In ENPH 253, we use transistors as switches to turn on and off larger amounts of current.


Two major types of transistors:

- Bipolar Junction Transistors
- MOSFETs

38

Discrete devices: BJT


Bipolar Junction Transistors

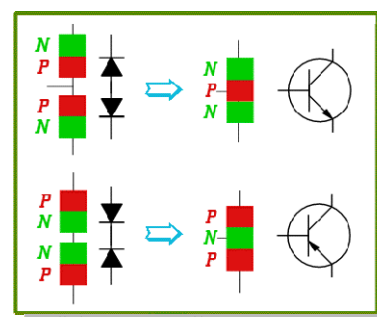

39

Discrete devices: BJT

Bipolar Junction Transistors

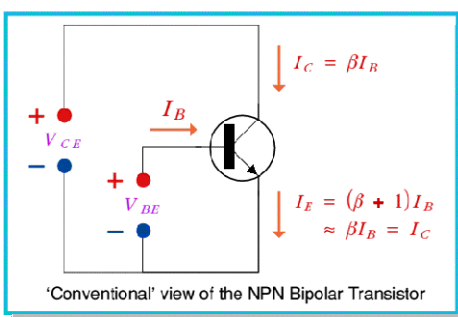

$I_C = \beta I_B$
 $I_E = (\beta + 1) I_B \approx \beta I_B = I_C$

'Conventional' view of the NPN Bipolar Transistor

40


Discrete devices: BJT

General Purpose Transistors

NPN Silicon

2N3903
2N3904*

*Metallized Preferred Device

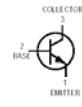

CASE 29-04, STYLE 1
TO-18 (TO-226AA)

Rating	Symbol	Value	Unit
Collector-Emitter Voltage	V_{CE}	40	Vdc
Collector-Base Voltage	V_{CB}	50	Vdc
Emitter-Base Voltage	V_{EB}	5.0	Vdc
Collector Current—Continuous	I_C	200	mAdc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/ $^\circ\text{C}$
Total Device Dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	1.5 12	Watts mW/ $^\circ\text{C}$
Operating and Storage Junction Temperature Range	T_j, T_{stg}	-55 to +150	$^\circ\text{C}$

41

Discrete devices: BJT

Bipolar Junction Transistors

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted) (Continued)

Characteristic	Symbol	Min	Max	Unit
ON CHARACTERISTICS				
DC Current Gain ⁽¹⁾ ($I_C = 0.1\text{ mAdc}$; $V_{CE} = 1.0\text{ Vdc}$)	β_{FE}	20	—	—
		40	—	—
($I_C = 1.0\text{ mAdc}$; $V_{CE} = 1.0\text{ Vdc}$)	β_{FE}	35	—	—
		70	—	—
($I_C = 10\text{ mAdc}$; $V_{CE} = 1.0\text{ Vdc}$)	β_{FE}	50	150	—
		100	300	—
($I_C = 50\text{ mAdc}$; $V_{CE} = 1.0\text{ Vdc}$)	β_{FE}	30	—	—
		60	—	—
($I_C = 100\text{ mAdc}$; $V_{CE} = 1.0\text{ Vdc}$)	β_{FE}	15	—	—
		30	—	—
Collector-Emitter Saturation Voltage ⁽¹⁾ ($I_C = 10\text{ mAdc}$; $I_B = 1.0\text{ mAdc}$) ($I_C = 50\text{ mAdc}$; $I_B = 5.0\text{ mAdc}$)	$V_{CE(sat)}$	—	0.2 0.3	Vdc
Base-Emitter Saturation Voltage ⁽¹⁾ ($I_C = 10\text{ mAdc}$; $I_B = 1.0\text{ mAdc}$) ($I_C = 50\text{ mAdc}$; $I_B = 5.0\text{ mAdc}$)	$V_{BE(sat)}$	0.65	0.85 0.95	Vdc

42

Discrete devices: Transistors (NPN)

Build a circuit that :

- Uses a 3904 (NPN) transistor to light a lamp
- ❖ Check: when the 3904 is turned on, the Base-Emitter voltage should be ~ 0.7V
- ❖ Limit the current into the base!!
- ❖ Note: arrange the 3904 so the emitter voltage to ground does not change when the lamp is lit (it needs to be stable as a reference for the base voltage)

Discrete devices: Transistors (NPN)

Bipolar Junction Transistors

Typical circuit (NPN):
When S1 is closed, lamp lights up.

$I_B = (5-0.7)/1k = 4.3 \text{ mA}$
 $\beta = 30$
 $I_C = (30)4.3 \text{ mA} = 130 \text{ mA}$

$V_{BE} = 0.7 \text{ V}$
 $V_{CE} = 0.3 \text{ V}$

Checking V_{BE} is a quick way to test a transistor. If $V_{BE} \gg 0.7 \text{ V}$, the transistor is dead.

44

Discrete devices: Transistors (PNP)

Build a circuit that :

- Uses a 3906 (PNP) transistor to light a lamp
- ❖ Check: when the 3906 is turned on, the Base-Emitter voltage should be ~ 0.7V
- ❖ Note: arrange the 3906 so the emitter voltage to ground does not change when the lamp is lit (it needs to be stable as a reference for the base voltage)

Discrete devices: Transistors (PNP)

Bipolar Junction Transistors

Typical circuit (PNP):
When S2 is closed, lamp lights up.

46

Discrete devices: FETs

Field Effect Transistors

Gate voltage either ENHANCES or DEPLETES the conduction channel.

JFET = Junction FET
MOSFET = Metal Oxide Semiconductor FET

MOSFETs have an insulating layer at gate so draw less current.

Current passing from source to drain now controlled by VOLTAGE at the gate (rather than by CURRENT into the base as in a BJT).

47

Discrete devices: FETs

Field Effect Transistors

There are FOUR kinds of MOSFETs:

Enhancement Mode: N type P type

Increasing V_{gs} increases I_d .

Depletion : Increasing V_{gs} decreases I_d

48

FAIRCHILD SEMICONDUCTOR
HUFA75321P3, HUFA75321S3S
 Data Sheet December 2001

35A, 55V, 0.034 Ohm, N-Channel UltraFET Power MOSFETs

UltraFET These N-Channel power MOSFETs are manufactured using the innovative UltraFET[®] process. This advanced process technology achieves the lowest possible on-resistance per silicon area, resulting in outstanding performance. This device is capable of withstanding high energy in the avalanche mode and the diode exhibits very low reverse recovery time and stored charge. It was designed for use in applications where power efficiency is important, such as switching regulators, switching converters, motor drivers, relay drivers, low-voltage line switches, and power management in portable and battery-operated products.

Formerly developmental type 1A75321

Ordering Information

PART NUMBER	PACKAGE	BRAND
HUFA75321P3	TO-252AB	PL321P
HUFA75321S3S	TO-252AB	PL321S

NOTE: When ordering, use the entire part number. Add the suffix T to denote the TO-252AB variant in tape and reel, e.g., HUFA75321S3ST.

Packaging

JEDEC TO-252AB JEDEC TO-252AB

49

Discrete devices: MOSFETS

Build a circuit that :

- Uses a MOSFET to light a lamp
- ❖ Note: no current is required to flow into the gate to switch on or off the MOSFET
- ❖ Make this circuit for both N and P type FETs

Discrete devices: MOSFETS

Enhancement: N type P type

51

Discrete devices: MOSFETS

If after closing S1 (and turning on the LED) we cut the circuit at the red line:

1. The LED will stay lit
2. The LED will go off

52

Things to keep in mind for Lab 1

- Bring a Lab Notebook!
- Circuit (LM311) and TINAH are not connected to a common ground.
- The LM311 comparator output pin is not pulled up.
- The power rail break in the proto board is not bridged.
- The strobe pin of the LM311 is pulled low.
- The ground pin of the LM311 is not grounded.
- Blowing up the TINAH. Please use LM311 to interface to the frequency generator.

53